

# Logic Synthesis & Verification, Fall 2025

National Taiwan University

## Programming Assignment 1


2 (b)

- `read_blif`、`print_stats`

```
abc 01> read alu.blif
abc 02> print_stats
alu          : i/o =   5/   3  lat =   0  nd =   8  edge =   18  cube =   20  lev =  3
```


- `show`

 The network contains 8 logic nodes and 0 latches.




- `strash \show`

 The network contains 30 logic nodes and 0 latches.



- `collapse \show_bdd -g`

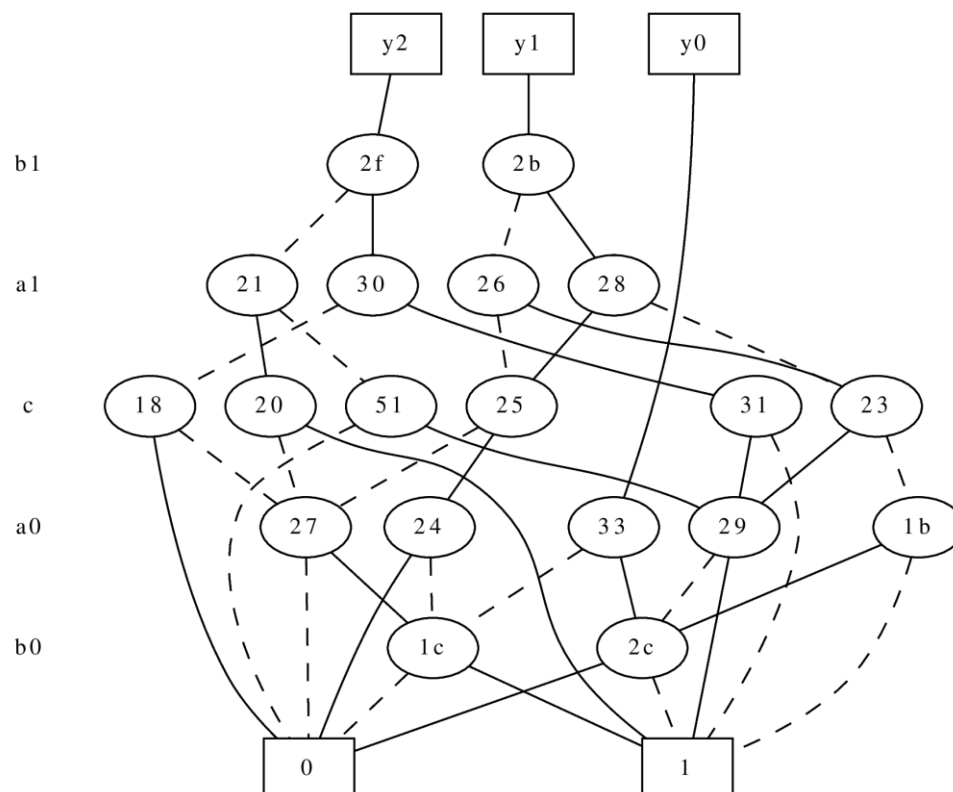

### 3 (a)

1. After running `aig`, the circuit still contains SOP nodes, showing only 8 logic nodes with depth 3, and it only reports that 30 AND gates would be required if expanded.

After running `strash`, the network is fully converted into an AIG with 30 AND nodes and depth 10.

Therefore, `aig` provides a higher-level AIG view, while `strash` performs the full structural hashing to obtain the true AIG representation.

```
abc 11> read alu.blif
abc 12> aig
abc 12> print_stats
alu          : i/o =   5/   3 lat =   0 nd =   8 edge =   18 aig =   30 lev = 3
abc 12> strash
abc 13> print_stats
alu          : i/o =   5/   3 lat =   0 and =   30 lev = 10
```

2. `bdd` produces separate BDDs, while `collapse` creates a collapsed BDD with reduced size and depth.

```
abc 13> read alu.blif
abc 14> bdd
abc 14> print_stats
alu          : i/o =   5/   3 lat =   0 nd =   8 edge =   18 bdd =   20 lev = 3
abc 14> collapse
abc 15> print_stats
alu          : i/o =   5/   3 lat =   0 nd =   3 edge =   12 bdd =   18 lev = 1
```

### 3 (b)

`read alu.blif; strash; collapse; sop`

```
abc 15> read alu.blif
abc 16> print_stats
alu          : i/o =   5/   3 lat =   0 nd =   8 edge =   18 cube =   20 lev = 3
abc 16> strash
abc 17> print_stats
alu          : i/o =   5/   3 lat =   0 and =   30 lev = 10
abc 17> collapse
abc 18> print_stats
alu          : i/o =   5/   3 lat =   0 nd =   3 edge =   12 bdd =   18 lev = 1
abc 18> sop
abc 18> print_stats
alu          : i/o =   5/   3 lat =   0 nd =   3 edge =   12 cube =   19 lev = 1
```

The network contains 3 logic nodes and 0 latches.

