

LSV PA1 Report

r13943063 陳立強

2 [Using ABC]

(b)

1. read the BLIF file into ABC (command “read”)

```
=====
abc 01> read comp.blif
abc 02> █
```


2. check statistics (command “print stats”)

```
abc 02> print_stats
comp : i/o = 5/ 3 lat = 0 nd = 3 edge = 15 cube = 42 lev = 1
```

 3. visualize the network structure (command “show”)

Network structure visualized by ABC
Benchmark "comp". Time was Fri Sep 13 21:44:12 2024.

The network contains 3 logic nodes and 0 latches.




4. convert to AIG (command “strash”)

```
abc 02> strash
abc 03> █
```

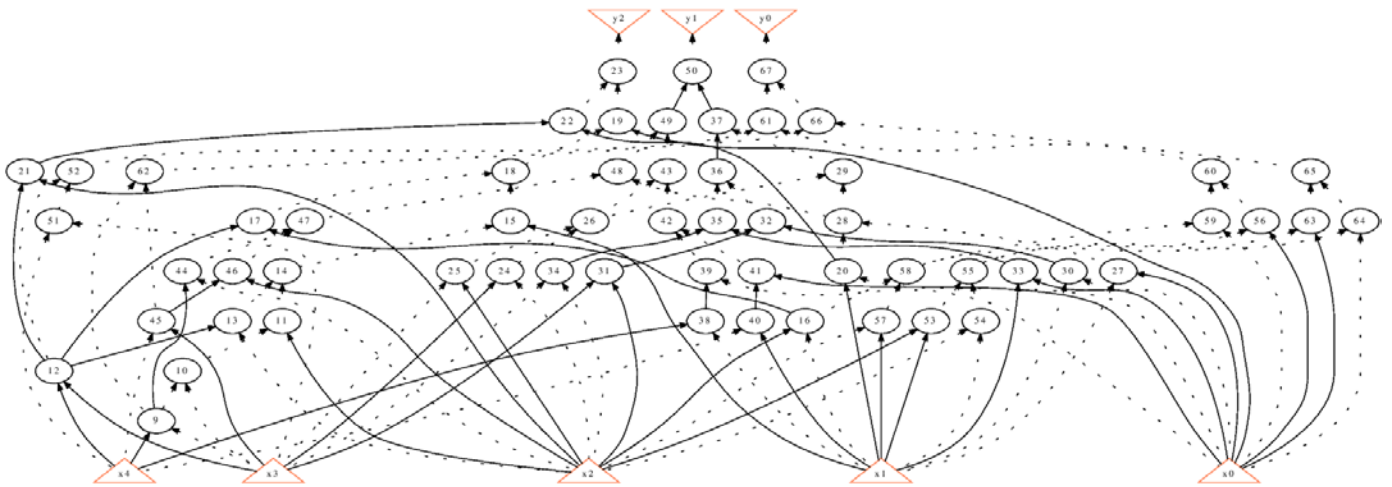5. visualize the AIG (command “show”)

Network structure visualized by ABC
Benchmark “comp”. Time was Fri Sep 13 22:53:42 2024.


The network contains 59 logic nodes and 0 latches.



6. convert to BDD (command “collapse”)

```
abc 03> collapse
abc 04>
```

 7. visualize the BDD (command “show bdd -g”; note that “show bdd” only shows the first PO; option “-g” can be applied to show all POs)



3 [ABC Boolean Function Representations]


(a) 1.

By command “aig”, we can see that the network structure showed below is still the same as the original one, this command converts node functions to AIG.

```
abc 02> aig
abc 02> print_stats
comp : i/o = 5/ 3 lat = 0 nd = 3 edge = 15 aig = 65 lev = 1
```

Network structure visualized by ABC
Benchmark "comp". Time was Wed Sep 18 15:29:47 2024.

 The network contains 3 logic nodes and 0 latches.




By command “strash”, it transforms combinational logic into an AIG, with structurally hashed.

```
strash
abc 03> print_stats
comp : i/o = 5/ 3 lat = 0 and = 59 lev = 8
```


Network structure visualized by ABC
Benchmark "comp". Time was Fri Sep 13 23:17:37 2024.

 The network contains 59 logic nodes and 0 latches.



By command “bdd”, we can see that the result is the same as command “collapse”.
 
```
collapse
abc 03> print_stats
comp          : i/o =   5/   3  lat =   0  nd =   3  edge =   15  bdd =   21  lev = 1
```



(b)

Use command “logic” to transforms the AIG into a logic network with the SOP representation of the two-input AND-gates.

```
abc 01> read blif comp.blif
abc 02> strash
abc 03> print_stats
comp          : i/o = 5/ 3 lat = 0 and = 59 lev = 8
abc 03> logic
abc 04> print_stats
comp          : i/o = 5/ 3 lat = 0 nd = 59 edge = 118 cube = 59 lev = 8
abc 04> show
```

Network structure visualized by ABC
Benchmark "comp". Time was Wed Sep 18 17:04:19 2024.

The network contains 59 logic nodes and 0 latches.

